
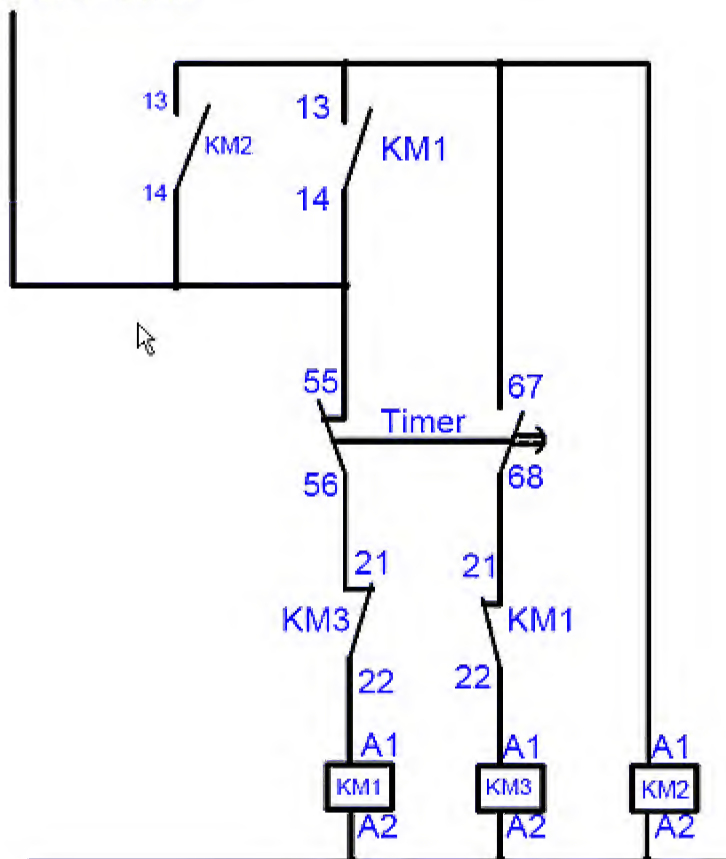


From 96 on overload

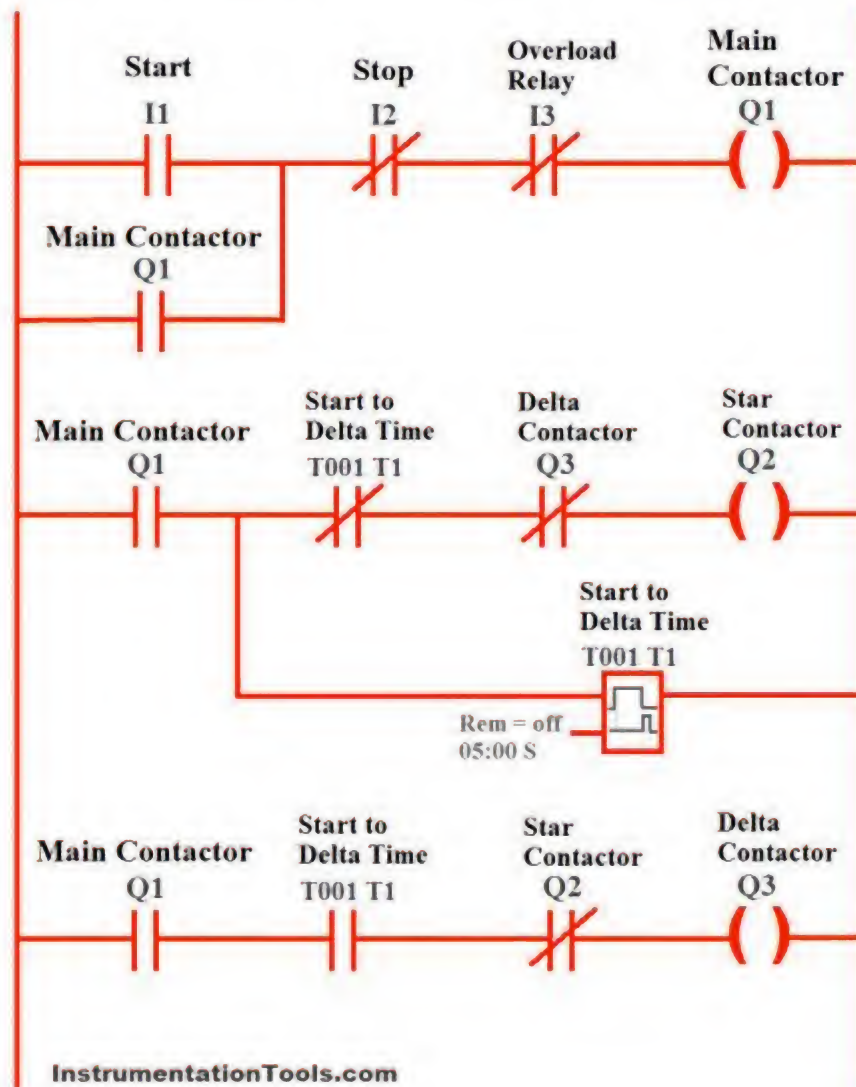

STAR-DELTA MOTOR STARTER LADDER LOGIC



Application example

Control and power circuit for star-delta starter

